

VISER- Master Elektrotehničko Inženjerstvo,
Projektovanje Elektroenergetskih Pretvarača (PEEP)- II kolokvijum-REŠENJA ZADATAKA

1. ZADATAK:


Potrebno je nacrtati električnu šemu i projektovati AC/DC električni neizolovani pretvarač napona za koji su dati ulazni podaci za projektovanje:

- Nominalni ulazni napon $230V \pm 10\%$, 50Hz
- Izlazni napon 110VDC
- Izlazna snaga 1.1kW
- Talasnost struje prigušnice $\leq 25\%$
- Talasnost izlaznog napona $\leq 0.5\%$
- Radna učestanost 50kHz

- Dimenzionisati prekidačke elemente prema struji i naponu (prema MAX naponu koji moraju izdržati i prema srednjoj vrednosti struje)
- Zanemariti padove napona i komutacione gubitke na prekidačkim elementima, kao i unutrašnje otpornosti pasivnih elemenata. Smatrati da je opterećenje na izlazu približno konstantno

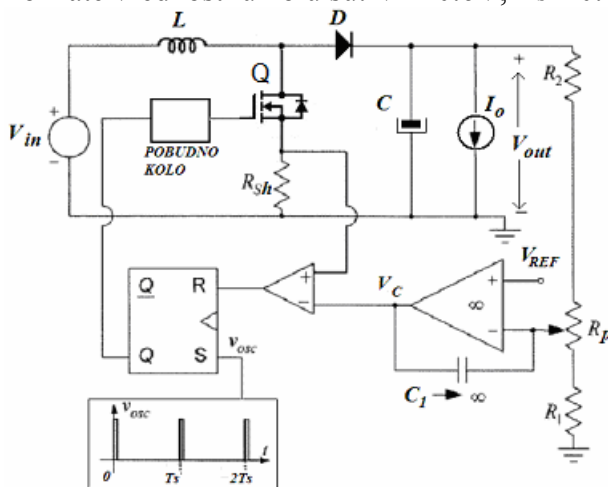2. ZADATAK:

Upravljačkim kolom DC/DC pretvarača sa slike se obezbeđuje konstantna vrednost izlaznog napona od 250VDC na opterećenju snage 1.1kW, za vrednost ulaznog DC napona $110V \pm 10\%$. Perioda vrlo uskih kratkotrajnih impulsa oscilatora iznosi $T_s = 25\mu s$. Prekidački tranzistor je idealnih karakteristika. Poznate vrednosti u kolu su: $V_D = 0.6V$, $R_{sh} = 0.1\Omega$, $L = 150\mu H$. Naponska referenca iznosi $V_{ref} = 5V$.




- A) Ispitati u kom režimu radi pretvarač obzirom na struju prigušnice za ceo opseg ulaznog napona
- B) U kom opsegu se menja talasnost struje prigušnice L
- C) Proračunati razdelnik R_1 - R_p - R_2 u povratnoj sprezi po naponu
- D) Proračunati vrednost kondenzatora C ako je zahtevana talasnost izlaznog napona $\leq 5\%$
- E) Za maksimalnu vrednost ulaznog napona nacrtati vremenske talasne oblike, struja: prigušnice L, prekidačkog tranzistora Q, diode D i napona: na izlazu flip-flopa, na otpornom šantu R_{sh} , kontrolnog napona V_C , u toku jedne periode u ustaljenom stanju

3. ZADATAK:

U kolu u zadatku 1 potrebno je LEM strujnim modulom meriti trenutnu vrednost struje prekidačkog tranzistora na osciloskopu. Na raspolaganju su LEM strujni senzori prenosnog odnosa 1:10000, napona napajanja $\pm 15V$ DC, ali različitih propusnih opsega 1MHz, 10MHz i 50MHz i opsega struja 10A, 25A, 50A, 100A. Povraćeno naelektrisanje diode kod isključenja je $Q_{rr} = 1\mu C$. Vreme oporavka diode je $t_{rr} = 100ns$. Odabrati potreban LEM senzor, nacrtati šemu merenja struje i dimenzionisati merni otpornik na izlazu LEM modula tako da se na njemu obezbedi naponski signal 0-10VDC koji se vodi na ulaz osciloskopa radi merenja. Vršnu vrednost struje diode (tzv. "strujni pik") računati prema formuli $I_{RM} \approx 2Q_{rr}/t_{rr}$.

↑ ZADATAC

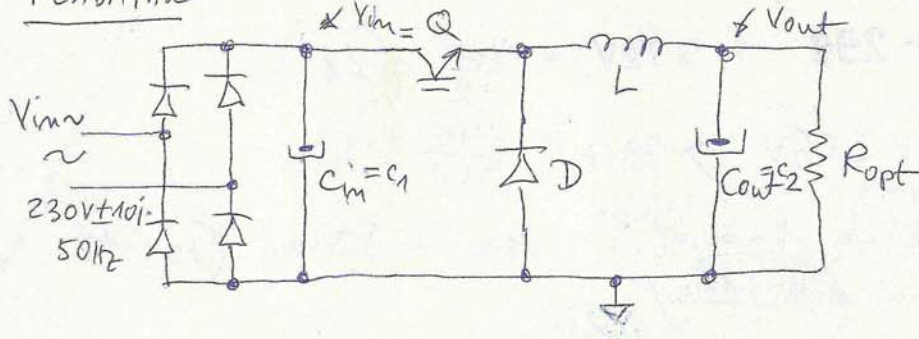

①

$$P_{out} = 1,1 \text{ kW}$$

$$\Delta L_o = \Delta L_i \leq 25\%$$

$$\Delta V_{out} \leq 0,5\%$$

$$f_{sw} = 50 \text{ kHz}$$

$$T = \frac{1}{f_{sw}} = \frac{1}{50 \cdot 10^3} = 20 \mu\text{s}$$

$P_{in} \approx P_{out}$ (zanem. izgubitve na Q, D)

$$V_{in, \max} = 230\text{V} + 10\% = 1,1 \cdot 230\text{V} = 253\text{V AC}$$


$$V_{in, \max} = 253\text{V AC}$$

$$V_{in, \min} = 230\text{V} - 10\% = 0,9 \cdot 230\text{V} = 207\text{V AC}$$

$$V_{in, \min} = 207\text{V AC}$$

$$207\text{V AC} \leq V_{in} \leq 253\text{V AC}$$

$$V_{in} = V_{in, DC}$$

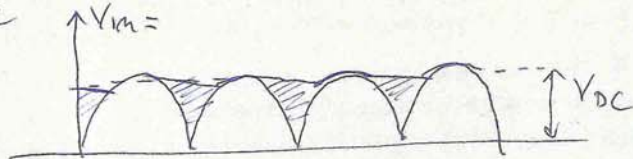

* Diskusija za $C_m = C_1$

$$R_{ew} = \frac{V_{in, DC}}{I_{in, DC}}$$

$$\frac{\Delta V}{V_{DC}} = 2 \cdot \frac{1}{4f \cdot R_{ew} \cdot C_1 - 1}$$

$$V_{in, DC} = V_m \cdot \frac{4f \cdot R_{ew} \cdot C_1 - 1}{4f \cdot R_{ew} \cdot C_1}$$

$$\frac{\Delta V}{V_{DC}} = \frac{2}{4f \cdot R_{ew} \cdot C_1 - 1} = \frac{2}{4f \cdot \frac{V_{in, DC}}{I_{in, DC}} \cdot C_1 - 1}$$

$$\left(\frac{\Delta V}{V_{DC}} \right) \leq 10\%$$

UVRABIANJE

$$\frac{2}{4f \cdot \frac{V_{in, DC}}{I_{in, DC}} \cdot C_1 - 1} = 0,1 \Rightarrow f \cdot \frac{V_{in, DC}}{I_{in, DC}} \cdot C_1 - 1 = \frac{2}{0,1}$$

$$4f \cdot V_{in, DC} \cdot \frac{C_1}{I_{in, DC}} = 20 + 1$$

$$4f \cdot V_{in, DC} \cdot \frac{C_1}{I_{in, DC}} = 21 \quad f = 50 \quad V_{in, DC} \approx 325\text{V}$$

$$\frac{C_1}{I_{in, DC}} \approx \frac{21}{325 \cdot 50 \cdot 4} = 0,0013/4$$

$$\text{za } I_{in, DC} = 1\text{A} \quad C_1 \approx \frac{1300}{4} \mu\text{F} \quad \left\{ \begin{array}{l} 1\text{A} \rightarrow \frac{1300}{4} \mu\text{F} \end{array} \right\} = 325 \mu\text{F}$$

$$* \text{ ZA } \left(\frac{\Delta V}{V_{DC}} \right) \leq 15\%$$

$$\frac{C_1}{I_{inoc}} \approx \frac{14,33}{325 \cdot 50 \cdot 4} = 0,0009 \approx 0,001/4$$

(2)

$$\text{ZA } I_{inoc} = 1A \quad C_1 \approx \frac{1000}{4} \mu F \Rightarrow 1A \rightarrow \frac{1000}{4} \mu F$$

Alio uslovima DA ZA $1A \rightarrow \frac{1000}{4} \mu F$ (2500μF)

$$* \text{ ZA } \frac{\Delta V}{V_{DC}} \leq 1\% \quad \frac{C_1}{I_{inoc}} \approx \frac{0,013}{4} \Rightarrow I_{inoc} = 1A \quad C_1 = \frac{13000}{4} \mu F$$

$$C_1 = 3250 \mu F$$

$$I_{inoc} \approx \frac{1100W}{324,3V} = 3,4A \rightarrow C_1 = 3,4 \cdot 1300 \mu F = 4420 \mu F$$

$$\text{uslovima} \quad C_{in} = C_1 = 4700 \mu F \quad \text{TAJDA ZA } \frac{\Delta V}{V_{DC}} \approx \frac{2}{450 \cdot 95 \cdot 4700 \mu F - 1}$$

- maksimalni inverz. napon na diodama

$$\text{u GRC ispravljaču je } \sqrt{2} \cdot V_{inmax} = \sqrt{2} \cdot 253 = 356,8V$$

uslovima se diode D1...D4 ZA

inverzni napon od $2 \cdot 356,8 = 713,6V$

uslovima diode ZA 800V

$$I_{SRD_{1-4}} \approx 15A \rightarrow$$

$$800V/15A$$

$$207\sqrt{2} \leq V_{inoc} \leq 253\sqrt{2}$$

$$\frac{\Delta V}{V_{DC}} = \frac{2}{450 \cdot 95 \cdot 4700 \mu F - 1}$$

$$\frac{\Delta V}{V_{DC}} = \frac{2}{4223-1} = \frac{2}{88,2}$$

$$\frac{\Delta V}{V_{DC}} \leq 0,0226$$

$$\left(\frac{\Delta V}{V_{DC}} \right) \leq 2,26\%$$

$$\delta = \frac{V_{out}}{V_{in}}$$

$$\delta_{max} = \frac{V_{out}}{V_{inocmin}} = \frac{110}{291,87} = 0,376$$

$$\delta_{min} = \frac{V_{out}}{V_{inocmax}} = \frac{110}{356,73} = 0,308$$

$$0,308 \leq \delta \leq 0,376 \quad 292V \leq V_{inoc} \leq 356,73V$$

L se dimensionuje ZA MAX ML. NAPON T. δ_{min}
 - kritična induktivnost

(3)

$$I_{out} = P_{out}/V_{out} = 1100/110 = 10A$$

$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{110V}{10A} = 11\Omega$$

$$L_c = \frac{1 - \delta_{min}}{2 f_{sw}}, R_{out} = ?$$

$$L_c = \frac{1 - 0,308}{2 \cdot 50 \cdot 10^3} \cdot 11 = 76 \mu H \xrightarrow{\text{usmeno}} 100 \mu H$$

$$I_{Lsr} = I_{out} = 10A \quad \Delta i_L = \frac{\Delta i_L \%}{100} \cdot I_{Lsr} = \frac{25}{100} \cdot 10 = 2,5A$$

$$L \cdot \Delta i_L = (V_{inmax} - V_{out}) \cdot \delta_{min} = (V_{inmax} - V_{out}) \cdot \delta_{min} \cdot T = \frac{V_{inmax} - V_{out}}{f_{sw}}$$

$$L \cdot \Delta i_L = (V_{inmax} - V_{out}) \cdot \frac{\delta_{min}}{f_{sw}} \quad \Delta i_L \leq 2,5A$$

$$L \geq \frac{(V_{inmax} - V_{out}) \delta_{min}}{f_{sw} \cdot \Delta i_L} = \frac{356,8 - 110}{50 \cdot 10^3 \cdot 2,5} \cdot 0,308$$

$$L \geq 608,11 \mu H \xrightarrow{\text{usmeno}} L^* = 610 \mu H$$

KADA SE NAPON V_{DC} POKRETA (291,87V) PRI $L^* = 610 \mu H$

$$\Delta i_L = \frac{V_{inmin} - V_{out}}{L^*} \cdot \frac{\delta_{max}}{f_{sw}} = \frac{291,87 - 110}{610 \mu H \cdot 50 \cdot 10^3} \cdot 0,376$$

$$\Delta i_L = 2,24A < 2,5A \quad \checkmark$$

$$C_2 = \frac{1 - \delta_{min}}{8 \cdot L^* \cdot f_{sw}^2 \left(\frac{\Delta V_{out}}{V_{out}} \right)} = \frac{1 - 0,308}{8 \cdot 610 \mu \cdot (50 \cdot 10^3)^2 \cdot \frac{0,5}{100}}$$

$$C_2 = \frac{0,692 \cdot 100}{4,88 \cdot 10^{-3} \cdot 2500 \cdot 10^6 \cdot 0,5} = \frac{69,2}{12,2 \cdot 0,5} \cdot 10^{-6}$$

$$= 11,34 \mu F \xrightarrow{\text{usmeno}} C_2^* = 22 \mu F$$

$$\omega_{rez} = \frac{1}{\sqrt{L^* C_2^*}} = \frac{1}{\sqrt{610 \mu \cdot 22 \mu}} = 8,632 \cdot 10^3 \text{ rad/s}$$

$$\rightarrow f_{rez} = \frac{8,632 \cdot 10^3}{2\pi} = 1,374 \text{ kHz}$$

$$f_{sw} \gg f_{rez}$$

2201574

4

$$V_{out} = 250V DC. \quad P_{out} = 1,1kW \quad V_{in} = 110V \pm 10\%$$

$$T_s = 25\mu s \rightarrow f_{sw} = 40kHz \quad R_{sk} = 0,1V$$

$$L = 150\mu H. \quad V_{ref} = 5V$$

$$a) \quad I_{msr} \geq \frac{V_{in}}{2L \cdot f_s} \left(1 - \frac{V_{in}}{V_{out}}\right) \quad V_{inmin} = 110 - 11V = 99V$$

$$V_{inmax} = 110 + 11 = 121V$$

$$99V < V_{in} < 121V$$

$$\left. \begin{array}{l} V_{out} = 250V DC \\ P_{out} = 1100W \end{array} \right\} I_{out} = \frac{1100}{250} = 4,4A$$

$$P_{in} \approx P_{out} \quad V_{inmin} \cdot I_{inmax} = 1100W \Rightarrow I_{inmax} = \frac{1100}{99} = 11,11A$$

$$V_{out} = \frac{V_{inmin}}{1-\delta} \Rightarrow \delta_{max} = 1 - \frac{V_{inmin}}{V_{out}} \quad I_{inmin} = 1100 \Rightarrow I_{inmin} = \frac{1100}{121} = 9,1A$$

$$\delta_{max} = 0,604 \quad I_{inmin} = 9,1A$$

$$I_{inmax} > \frac{V_{inmin}}{2L \cdot f_s} \left(1 - \frac{V_{inmin}}{V_{out}}\right) = \frac{99}{2 \cdot 150\mu \cdot 40 \cdot 10^3} \left(1 - \frac{99}{250}\right) = 4,98A$$


$$0,604 = \delta_{max}$$

$11,11A > 4,98A \rightarrow$ konstruktor rezili

$$I_{inmin} > \frac{V_{inmax}}{2L \cdot f_s} \left(1 - \frac{V_{inmax}}{V_{out}}\right) = \frac{121}{2 \cdot 150\mu \cdot 40 \cdot 10^3} \left(1 - \frac{121}{250}\right) = 5,2A$$

$$0,516 = \delta_{min}$$

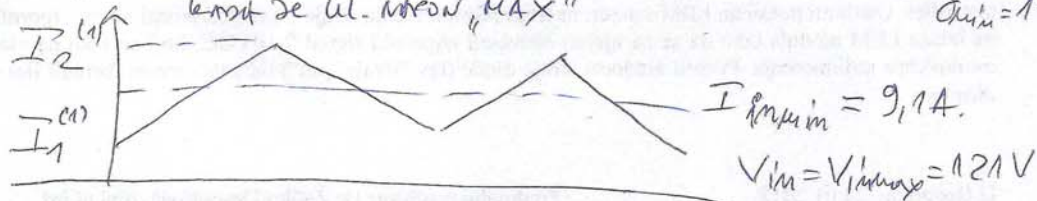6) $9,1A > 5,2A \rightarrow$ konstruktor rezili
kroz de ul. napon "MAX"




$$I_1^{(1)} + I_2^{(1)} = 2I_{inmin} = 18,2A$$

$$I_2^{(1)} - I_1^{(1)} = \frac{V_{inmax}}{L} \delta_{min} T = \frac{121}{150\mu} \cdot 0,516 \cdot \frac{1}{40 \cdot 10^3} = 10,46A$$


$$\begin{cases} I_1^{(1)} + I_2^{(1)} = 18,2 \text{ A} \\ -I_1^{(1)} + I_2^{(1)} = 10,46 \text{ A} \end{cases} \Rightarrow 2I_2^{(1)} = 28,66 \Rightarrow I_2^{(1)} = 14,33 \text{ A} \quad (5)$$
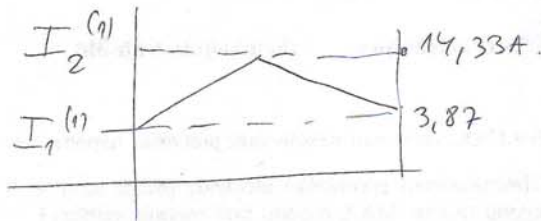
$$I_1^{(1)} = 18,2 - 14,33 = 3,87 \text{ A}$$



$$\Delta i_L = 10,46 \text{ A}$$

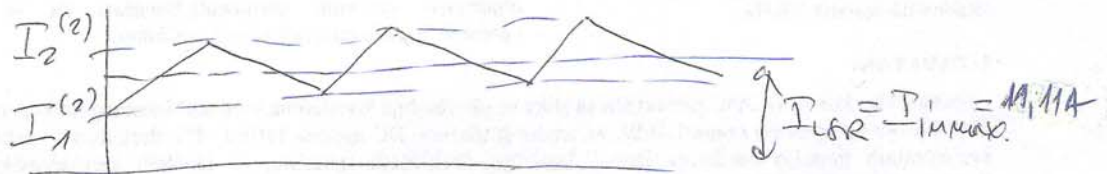kada se menja smer "min" $V_{in} = 99 \text{ V}$



$$I_1^{(2)} + I_2^{(2)} = 2 \cdot 11,11 \text{ A} = 22,22 \text{ A}$$


$$-I_1^{(2)} + I_2^{(2)} = \frac{V_{inmin}}{L} \cdot \Delta t_{max} \cdot T = \frac{99}{150 \mu} \cdot 9604 \cdot \frac{1}{40 \cdot 10^3}$$

$$= 9,966 \text{ A}$$

$$\begin{cases} I_1^{(2)} + I_2^{(2)} = 22,22 \text{ A} \\ -I_1^{(2)} + I_2^{(2)} = 9,966 \text{ A} \end{cases} \Rightarrow 2I_2^{(2)} = 32,186$$


$$I_2^{(2)} = 16,1 \text{ A}$$
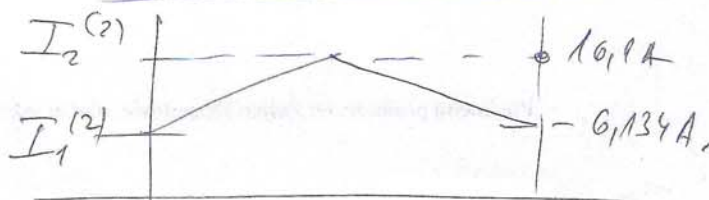
$$I_1^{(2)} = I_2^{(2)} - 9,966 = 6,134 \text{ A}$$



$$\Delta i_L = 9,96 \text{ A}$$
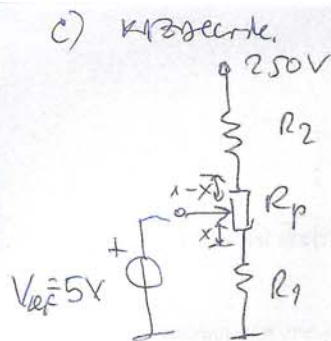
$$9,96 \text{ A} \leq \Delta i_L \leq 10,46 \text{ A}$$



$$\frac{250V}{5V} = 50$$

(6)

Nominalni prenosni odnos izlaza 1:50
 uslošno $R_1 = 1k$ $R_2 = 56k$.

$$\frac{V_{out}}{R_1 + R_2 + R_p} \cdot (R_1 + R_p \cdot x) = V_{ref}$$

$$\frac{R_1 + R_p \cdot x}{R_1 + R_2 + R_p} = \frac{1}{50} = 0,02. \quad \text{za } x = 0,5$$

$$R_1 + \frac{R_p}{2} = (R_1 + R_2 + R_p) \cdot 0,02 \Rightarrow R_1 + 0,5R_p = (R_1 + R_2) \cdot 0,02 + R_p \cdot 0,02$$

$$(R_1 + R_2) \cdot 0,02 - R_1 = 0,5R_p - 0,02R_p$$

$$57k \cdot 0,02 - 1k = 0,48R_p$$

$$1,14k - 1k = 0,48R_p \Rightarrow R_p = 291,66\Omega$$


* ici mi namo $R_p = 500\Omega$

$$R_1 + R_p \cdot x = \frac{1}{50} \cdot (R_1 + R_2 + R_p)$$

$$x = \frac{0,02(R_1 + R_2 + R_p) - R_1}{R_p} = \frac{0,02(57,5k) - 1k}{0,5k}$$

$$x = 0,3$$

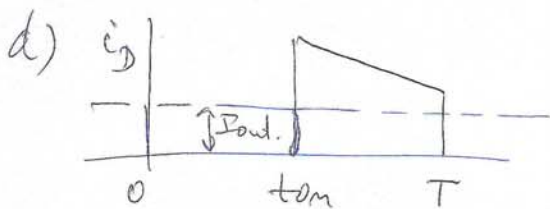$R_1 = 1k$ $R_2 = 56k$ $R_p = 500\Omega$ $x = 0,3$



(7)

$$I_{out} \cdot t_{on} = C \Delta V_{out}$$

$$I_{out} \cdot \frac{t_{on}}{T} = C \Delta V_{out} \cdot f$$

$$\frac{\Delta V_{out}}{V_{out}} \leq 5\% = 0,05$$

$$\Delta V_{out} = \frac{I_{out} \cdot \frac{t_{on}}{T}}{C f_{sw}}$$

$$\frac{\Delta V_{out}}{V_{out}} = \frac{I_{out} \cdot \delta}{C V_{out} f_{sw}} \leq 0,05$$

$$\delta = \delta_{max}$$

$$C \geq \frac{I_{out} \cdot \delta_{max}}{V_{out} \left(\frac{\Delta V}{V_{out}} \right) \cdot f_{sw}}$$


$$C \geq \frac{I_{out} \cdot \delta}{V_{out} \left(\frac{\Delta V_{out}}{V_{out}} \right) f_{sw}}$$

$$I_{out} = \frac{250W}{R_{out}}$$

$$I_{out} = \frac{1100W}{250V} = 4,4A$$

$$C \geq \frac{4,4 \cdot 0,604}{250 \cdot 0,05 \cdot 40 \cdot 10^3}$$
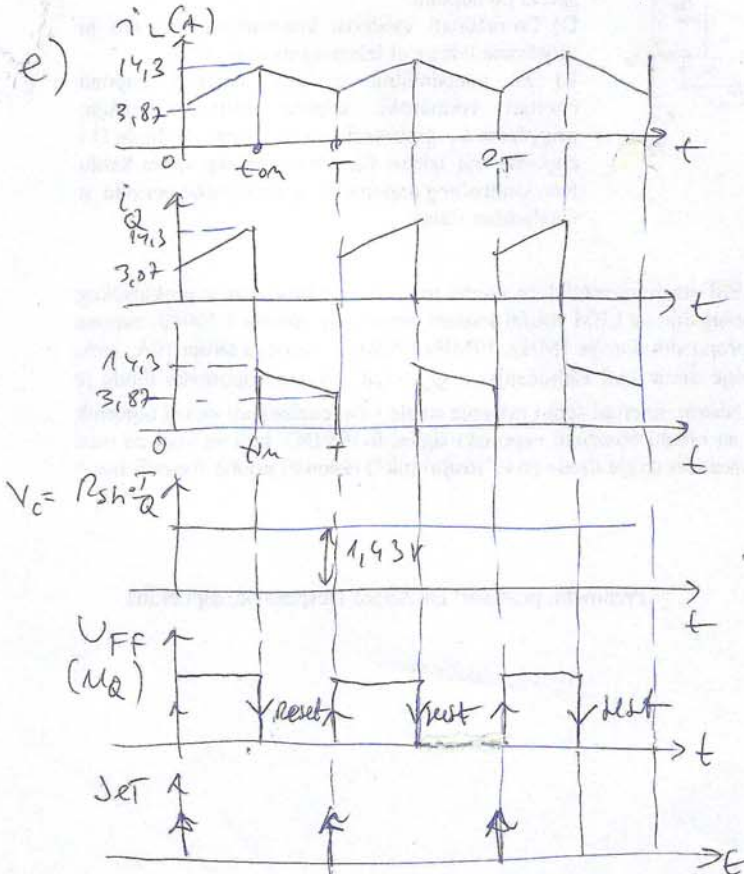
$$C \geq 5,31\mu F \rightarrow C_{out} = 10\mu F$$




$$\rightarrow \sim 100N \rightarrow C_1 \cdot V_{C1} = V_{ref} - V_C$$

$$V_{C1} = 5 - 1,43 = 3,57V$$

3 ZADANJE

8

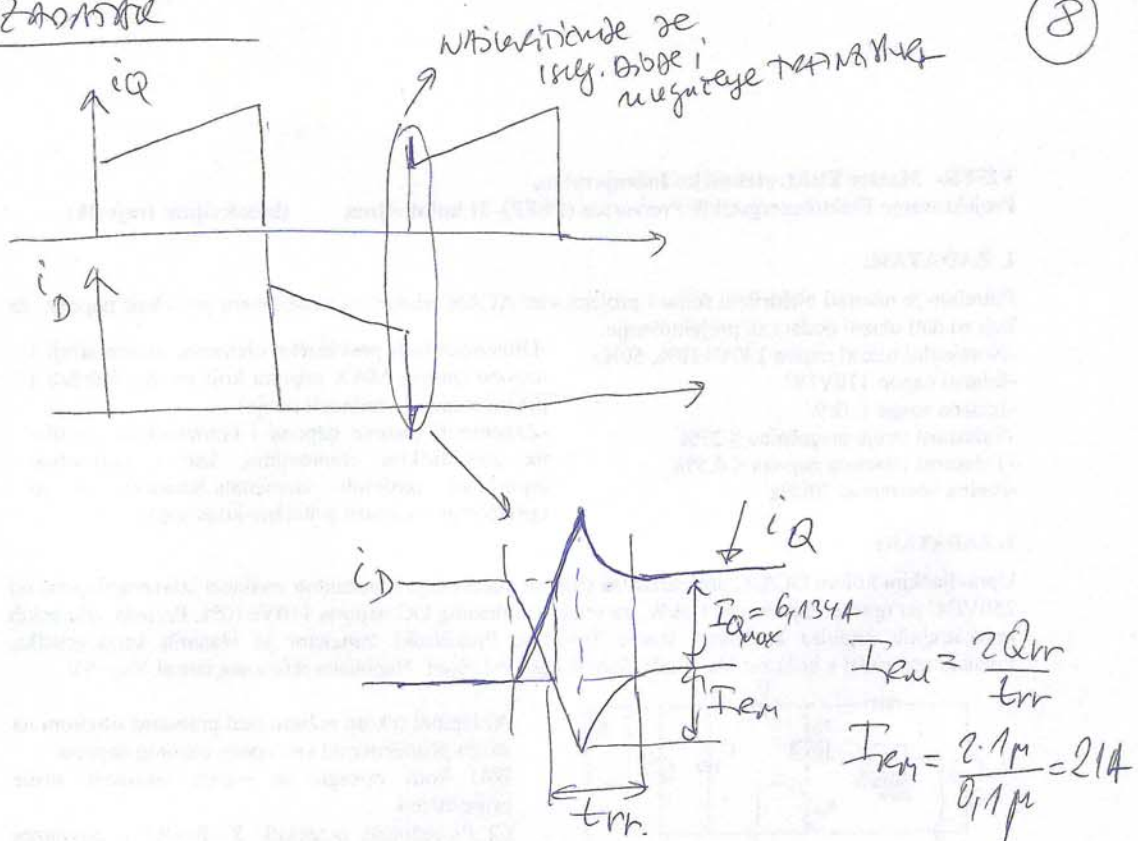

Našleđništvo; trenutni pik + $I_{Qmax} = I_{RM} + I_1^{(2)}$
 sumari

$$I_{pk} = 21 + 6,134 = 27,134A \rightarrow \text{našleđništvo}$$

LEM unosi 2A 50A i max prop. ovako 50mA/k.

$$R_m \left(\frac{50}{10000} \right) = 10V \Rightarrow R_m = \frac{10000 \cdot 10}{50} = 2k\Omega$$

$$R_m \cdot I_m^2 = P_{dis} = 2k\Omega \cdot (5mA)^2 = 905W$$

$$R_m = 2k\Omega / 0,25W$$