



Elektrotehnika (ASUV)

Vežbe 4

Kondenzatori



Elektrostatika-Kondenzatori

I.7.12. Veza kondenzatora prikazana na slici priključena je na napon $U_{AB} = 50 \text{ V}$. Kapacitivnosti kondenzatora su:


$$C_1 = 20 \text{ pF}, C_2 = 12 \text{ pF}, C_3 = 40 \text{ pF},$$

$$C_4 = 18 \text{ pF}, C_5 = 15 \text{ pF}.$$

a) Izračunati ekvivalentnu kapacitivnost veze C_e .

b) Izračunati napon U_1 na kondenzatoru C_1 .

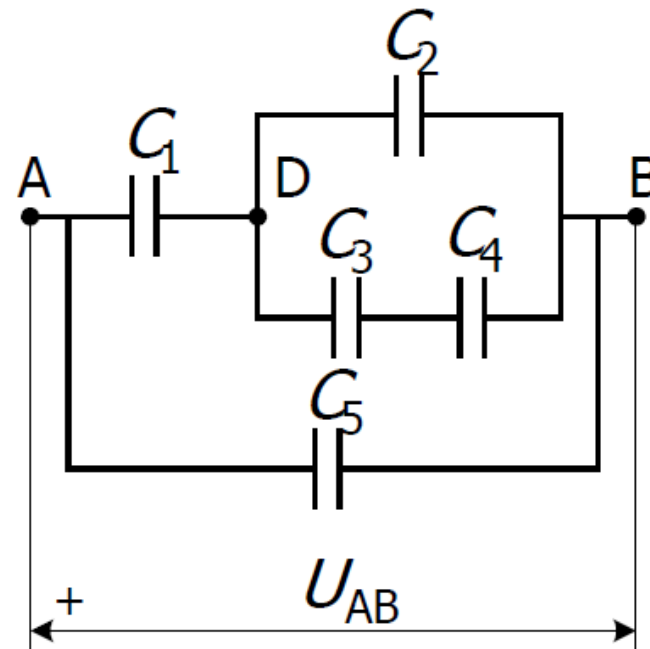c) Izračunati energiju W_{e4} kondenzatora C_4 .





Elektrostatika-Kondenzatori

$$\text{a)} \quad \frac{1}{C_{34}} = \frac{1}{C_3} + \frac{1}{C_4} \quad \Rightarrow \quad C_{34} = \frac{C_3 C_4}{C_3 + C_4} = \frac{40 \text{ pF} \cdot 18 \text{ pF}}{40 \text{ pF} + 18 \text{ pF}} = 12,41 \text{ pF}$$

$$C_{234} = C_2 + C_{34} = 12 \text{ pF} + 12,41 \text{ pF} = 24,41 \text{ pF}$$

$$\frac{1}{C_{1234}} = \frac{1}{C_1} + \frac{1}{C_{234}} \quad \Rightarrow \quad C_{1234} = \frac{C_1 C_{234}}{C_1 + C_{234}} = \frac{20 \text{ pF} \cdot 24,42 \text{ pF}}{20 \text{ pF} + 24,41 \text{ pF}} = 11 \text{ pF}$$

$$C_e = C_{12345} = C_{1234} + C_5 = 11 \text{ pF} + 15 \text{ pF} = 26 \text{ pF}$$



Elektrostatika-Kondenzatori

b)

$$Q_{1234} = Q_1 = Q_{234} = U_{AB} \cdot C_{1234} = 50 \text{ V} \cdot 11 \cdot 10^{-12} \text{ F} = 550 \text{ pC}$$

$$U_1 = U_{AD} = \frac{Q_1}{C_1} = \frac{Q_{1234}}{C_1} = \frac{550 \cdot 10^{-12} \text{ C}}{20 \cdot 10^{-12} \text{ F}} = 27,5 \text{ V}$$



Elektrostatika-Kondenzatori

c)

$$U_{DB} = U_{AB} - U_{AD} = 22,5 \text{ V}$$
$$Q_{34} = Q_3 = Q_4 = U_{DB} \cdot C_{34} = 22,5 \text{ V} \cdot 12,41 \text{ pF} = 279,22 \text{ pC}$$
$$W_{e4} = \frac{Q_4^2}{2C_4} = \frac{Q_{34}^2}{2C_4} = \frac{(279,22 \cdot 10^{-12} \text{ C})^2}{2 \cdot 18 \cdot 10^{-12} \text{ F}} = 2,16 \text{ nJ}$$



Elektrostatika-Kondenzatori


I.7.13. Za kolo na slici poznato je:

$$C_1 = 60 \mu\text{F}, C_2 = 15 \mu\text{F},$$

$$C_4 = 10 \mu\text{F}, C_5 = 30 \mu\text{F}, C_6 = 15 \mu\text{F}.$$

Napon na kondenzatoru C_6 je $U_6 = 5 \text{ V}$,
dok je elektrostatička energija kondenzatora C_4
 $W_{e4} = 45 \cdot 10^{-4} \text{ J}$.

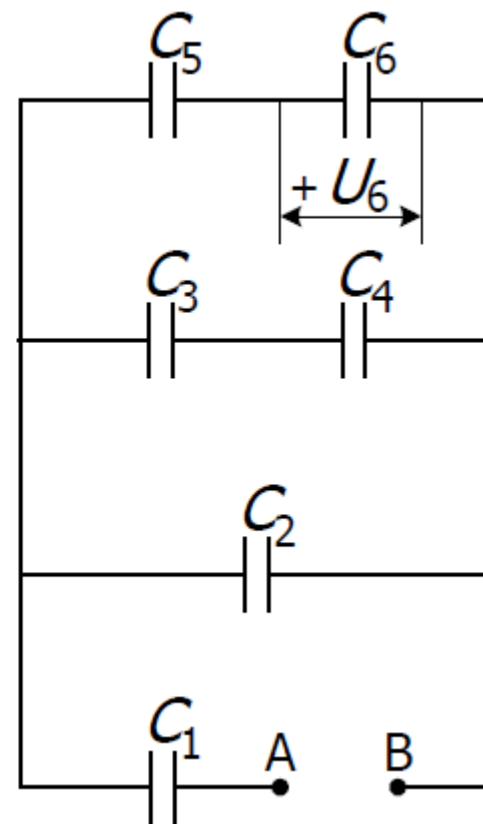- Odrediti kapacitivnost kondenzatora C_3 .
- Izračunati ekvivalentnu kapacitivnost veze C_e .
- Izračunati napon U_{AB} .






Elektrostatika-Kondenzatori

$$Q_6 = Q_5 = Q_{56} = U_6 \cdot C_6 = 40 \text{ V} \cdot 15 \cdot 10^{-6} \text{ F} = 600 \text{ } \mu\text{C}$$

$$U_5 = \frac{Q_5}{C_5} = \frac{Q_{56}}{C_5} = \frac{600 \cdot 10^{-6} \text{ C}}{30 \cdot 10^{-6} \text{ F}} = 20 \text{ V}$$

$$U_{DB} = U_5 + U_6 = 60 \text{ V}$$

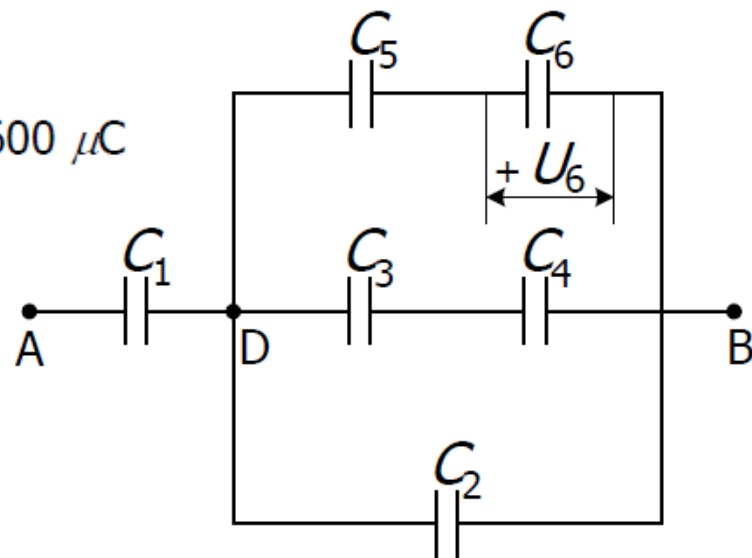

$$W_{e4} = \frac{1}{2} C_4 \cdot U_4^2 \quad \Rightarrow \quad U_4 = \sqrt{\frac{2W_{e4}}{C_4}} = \sqrt{\frac{2 \cdot 45 \cdot 10^{-4} \text{ J}}{10 \cdot 10^{-6} \text{ F}}} = 30 \text{ V}$$

$$Q_4 = C_4 \cdot U_4 = 10 \cdot 10^{-6} \text{ F} \cdot 30 \text{ V} = 300 \text{ } \mu\text{C}.$$



Elektrostatika-Kondenzatori

$$Q_3 = Q_4 = Q_{34} = 300 \mu\text{C}$$

$$U_3 = U_{AD} - U_4 = 30 \text{ V}$$

$$C_3 = \frac{Q_3}{U_3} = \frac{300 \cdot 10^{-6} \text{ C}}{30 \text{ V}} = 10 \mu\text{C}$$



Elektrostatika-Kondenzatori

$$\text{b)} \quad \frac{1}{C_{56}} = \frac{1}{C_5} + \frac{1}{C_6} \Rightarrow C_{56} = \frac{C_5 C_6}{C_5 + C_6} = \frac{30 \mu\text{F} \cdot 15 \mu\text{F}}{30 \mu\text{F} + 15 \mu\text{F}} = 10 \mu\text{F}$$

$$\frac{1}{C_{34}} = \frac{1}{C_3} + \frac{1}{C_4} \Rightarrow C_{34} = \frac{C_3 C_4}{C_3 + C_4} = \frac{10 \mu\text{F} \cdot 15 \mu\text{F}}{10 \mu\text{F} + 15 \mu\text{F}} = 5 \mu\text{F}$$

$$C_{23456} = C_2 + C_{34} + C_{56} = 15 \mu\text{F} + 5 \mu\text{F} + 10 \mu\text{F} = 30 \mu\text{F}$$

$$\frac{1}{C_e} = \frac{1}{C_{123456}} = \frac{1}{C_1} + \frac{1}{C_{23456}} \Rightarrow C_e = C_{123456} = \frac{C_1 C_{23456}}{C_1 + C_{23456}} = \frac{60 \mu\text{F} \cdot 30 \mu\text{F}}{60 \mu\text{F} + 30 \mu\text{F}} = 20 \mu\text{F}$$



Elektrostatika-Kondenzatori

$$c) \quad Q_{23456} = C_{23456} \cdot U_{DB} = 30 \cdot 10^{-6} \text{ F} \cdot 60 \text{ V} = 1800 \text{ } \mu\text{C}$$

$$Q_1 = Q_{23456} = 1800 \text{ } \mu\text{C}$$

$$U_{AD} = \frac{Q_1}{C_1} = \frac{Q_{23456}}{C_1} = \frac{1800 \cdot 10^{-6} \text{ C}}{60 \cdot 10^{-6} \text{ F}} = 30 \text{ V}$$

$$U_{AB} = U_{AD} + U_{DB} = 30 \text{ V} + 60 \text{ V} = 90 \text{ V}$$



Elektrostatika-Kondenzatori


I.7.14. Kapacitivnosti kondenzatora vezanih kao na slici su:

$$C_1 = 20 \mu\text{F}, C_2 = 20 \mu\text{F}, C_3 = 10 \mu\text{F},$$

$$C_4 = 15 \mu\text{F}, C_5 = 30 \mu\text{F}, C_6 = 10 \mu\text{F}.$$

Napon na kondenzatoru C_1 je $U_1 = 5 \text{ V}$.

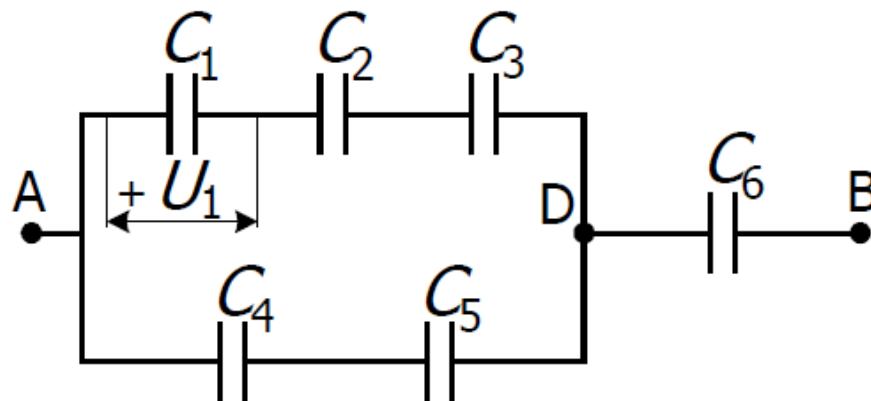- Izračunati ekvivalentnu kapacitivnost veze C_e .
- Izračunati napon U_{AB} , kao i napone i količine naelektrisanja svih kondenzatora.





Elektrostatika-Kondenzatori

$$a) \quad \frac{1}{C_{123}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = 0,05 \frac{1}{\mu F} + 0,05 \frac{1}{\mu F} + 0,1 \frac{1}{\mu F} = 0,2 \frac{1}{\mu F}$$

$$C_{123} = \frac{1}{0,2 \frac{1}{\mu F}} = 5 \mu F$$

$$\frac{1}{C_{45}} = \frac{1}{C_4} + \frac{1}{C_5} \Rightarrow C_{45} = \frac{C_4 C_5}{C_4 + C_5} = \frac{15 \mu F \cdot 30 \mu F}{15 \mu F + 30 \mu F} = 10 \mu F$$

$$C_{12345} = C_{123} + C_{45} = 5 \mu F + 10 \mu F = 15 \mu F$$

$$\frac{1}{C_e} = \frac{1}{C_{123456}} = \frac{1}{C_{12345}} + \frac{1}{C_6} \Rightarrow C_e = C_{123456} = \frac{C_{12345} C_6}{C_{12345} + C_6} = \frac{15 \mu F \cdot 10 \mu F}{15 \mu F + 10 \mu F} = 6 \mu F$$



Elektrostatika-Kondenzatori

$$\text{b)} \quad Q_1 = Q_2 = Q_3 = Q_{123} = U_1 \cdot C_1 = 5 \text{ V} \cdot 20 \cdot 10^{-6} \text{ F} = 100 \text{ } \mu\text{C}$$

$$U_2 = \frac{Q_2}{C_2} = \frac{Q_{123}}{C_2} = \frac{100 \cdot 10^{-6} \text{ C}}{20 \cdot 10^{-6} \text{ F}} = 5 \text{ V}$$

$$U_3 = \frac{Q_3}{C_3} = \frac{Q_{123}}{C_3} = \frac{100 \cdot 10^{-6} \text{ C}}{10 \cdot 10^{-6} \text{ F}} = 10 \text{ V}$$

$$U_{\text{AD}} = U_1 + U_2 + U_3 = 20 \text{ V}$$



Elektrostatika-Kondenzatori

$$Q_{45} = Q_4 = Q_5 = U_{AD} \cdot C_{45} = 20 \text{ V} \cdot 10 \cdot 10^{-6} \text{ F} = 200 \text{ } \mu\text{C}$$

$$U_4 = \frac{Q_4}{C_4} = \frac{Q_{45}}{C_4} = \frac{200 \cdot 10^{-6} \text{ C}}{15 \cdot 10^{-6} \text{ F}} = 13,33 \text{ V}$$

$$U_5 = \frac{Q_5}{C_5} = \frac{Q_{45}}{C_5} = \frac{200 \cdot 10^{-6} \text{ C}}{30 \cdot 10^{-6} \text{ F}} = 6,67 \text{ V}$$

$$Q_{12345} = Q_{123} + Q_{45} = 100 \text{ } \mu\text{C} + 200 \text{ } \mu\text{C} = 300 \text{ } \mu\text{C} = Q_6$$

$$U_6 = U_{DB} = \frac{Q_6}{C_6} = \frac{300 \cdot 10^{-6} \text{ C}}{10 \cdot 10^{-6} \text{ F}} = 30 \text{ V}$$

$$U_{AB} = U_{AD} + U_{DB} = 20 \text{ V} + 30 \text{ V} = 50 \text{ V}$$




Elektrostatika-Kondenzatori

I.7.15. Kondenzatori kapacitivnosti $C_1 = 10 \text{ pF}$, $C_2 = 20 \text{ pF}$ i $C_3 = 50 \text{ pF}$ vezani su u grupu kao na slici. Odrediti:


a) ekvivalentnu kapacitivnost veze C_e između tačaka A i B;

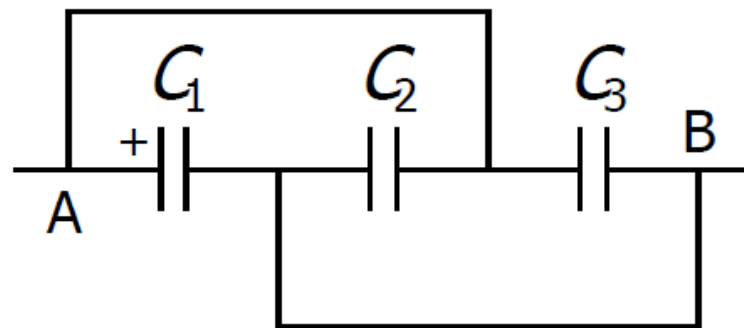b) napon U_{AB} ako je naelektrisanje na pozitivnoj elektrodi kondenzatora C_1 $Q_1 = 100 \text{ pC}$. Takođe odrediti količine naelektrisanja na kondenzatorima C_2 i C_3 .





Elektrostatika-Kondenzatori

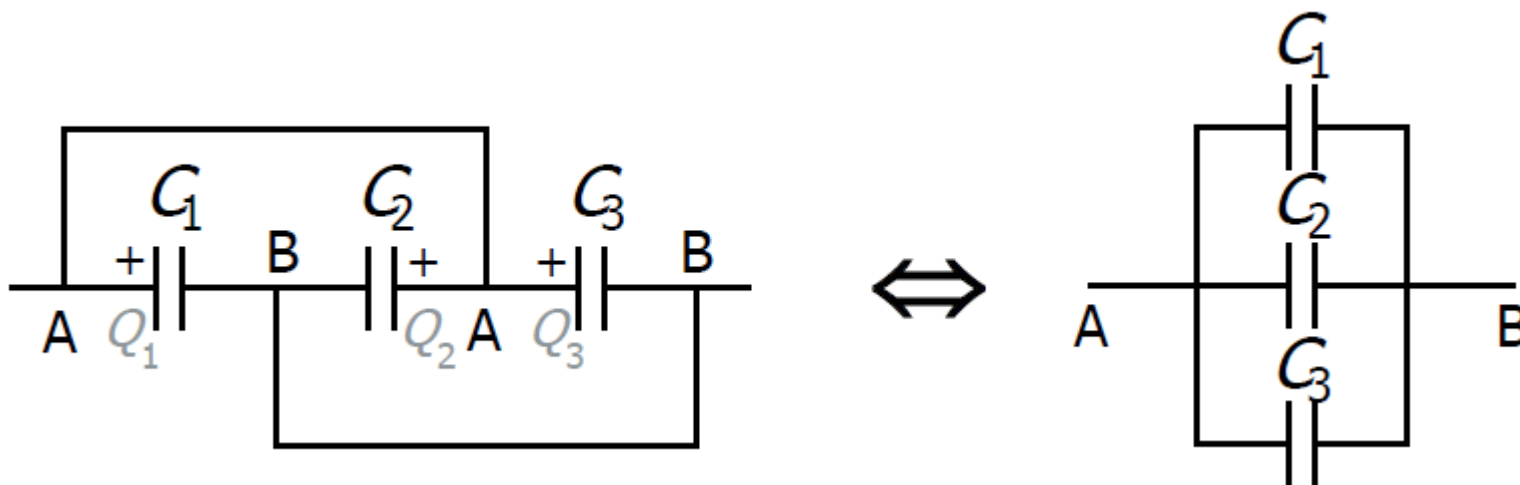

$$C_e = C_1 + C_2 + C_3 = 10 \text{ pF} + 20 \text{ pF} + 50 \text{ pF} = 80 \text{ pF}$$



Elektrostatika-Kondenzatori

b)

$$U_1 = U_{AB} = \frac{Q_1}{C_1} = \frac{100 \cdot 10^{-12} \text{ C}}{10 \cdot 10^{-12} \text{ F}} = 10 \text{ V}$$

$$Q_2 = U_{AB} \cdot C_2 = 10 \text{ V} \cdot 20 \cdot 10^{-12} \text{ F} = 200 \text{ pC}$$

$$Q_3 = U_{AB} \cdot C_3 = 10 \text{ V} \cdot 50 \cdot 10^{-12} \text{ F} = 500 \text{ pC}$$