



Elektrotehnika (AVT-ELITE)


Vežbe 6

Konturne struje vežbanje



Konturne struje

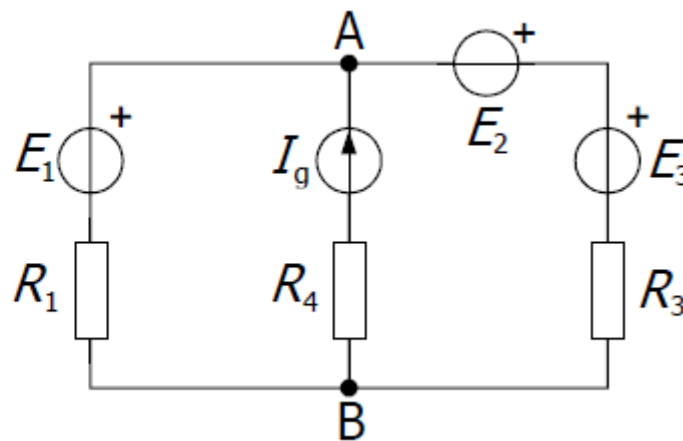II.8.2.3 Generatori $E_1 = 12\text{ V}$, $E_2 = 24\text{ V}$, $E_3 = 24\text{ V}$ i $I_g = 60\text{ mA}$, i otpornici $R_1 = 300\ \Omega$, $R_3 = 600\ \Omega$ i $R_4 = 500\ \Omega$ vezani su u kolo kao što je prikazano na slici. Metodom konturnih struja odrediti intenzitete struja u svim granama kola.





Konturne struje

Zadatak II.8.2.3

Rešenje:

$$n_g - (n_{\xi} - 1) - n_{I_g} = 1$$


$$R_{11}I_I + R_{12}I_{II} = E_I$$

$$I_{II} = I_g$$

$$R_{11} = R_1 + R_3 = 900 \, \Omega$$

$$R_{12} = R_3 = 600 \, \Omega$$

$$E_I = E_1 + E_2 - E_3 = 12 \, V$$

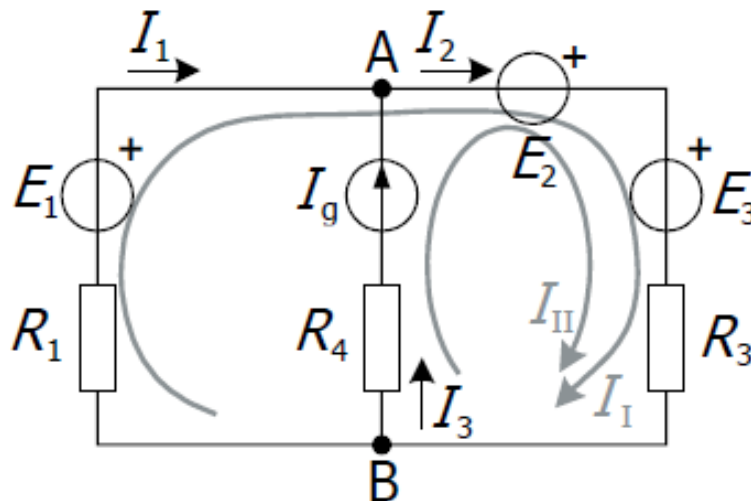




Konturne struje

Zadatak II.8.2.3

$$(R_1 + R_3)I_I + R_3I_{II} = E_1$$

$$I_{II} = I_g$$
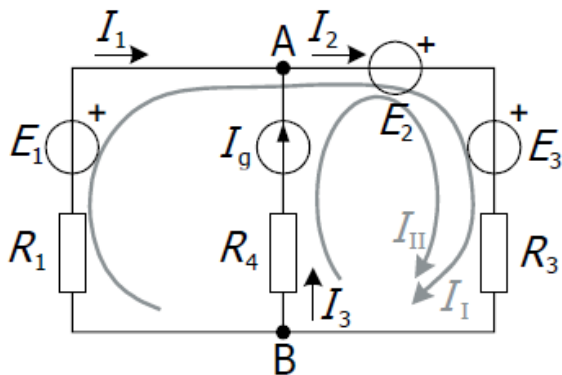
$$(R_1 + R_3)I_I + R_3I_g = E_1 \Rightarrow I_I = \frac{E_1 + E_2 - E_3 - R_3I_g}{R_1 + R_3} = \frac{-24 \text{ V}}{900 \Omega} = -0,0267 \text{ A} = -26,7 \text{ mA}$$



$$I_1 = I_I = -26,7 \text{ mA}, \quad I_2 = I_I + I_{II} = 33,3 \text{ mA}, \quad I_3 = I_{II} = I_g = 60 \text{ mA}$$



Konturne struje

II.8.2.4 U kolu na slici poznato je:


$$I_{g1} = 12 \text{ A}, I_{g2} = 6 \text{ A},$$

$$E_2 = 30 \text{ V}, E_3 = 20 \text{ V}, E_4 = 40 \text{ V},$$

$$R_1 = 10 \, \Omega, R_3 = 40 \, \Omega, R_4 = 20 \, \Omega, R_5 = 30 \, \Omega$$

a) Odrediti struje svih grana kola primenom metode konturnih struja.

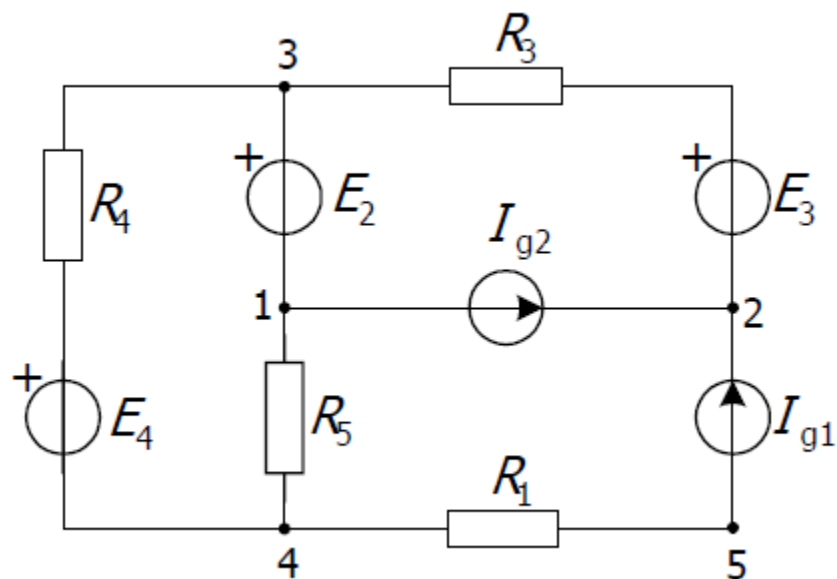b) Odrediti snagu strujnog generatora I_{g1} .





Konturne struje

Zadatak II.8.2.4 a)

$$n_g - (n_{\check{c}} - 1) - n_{I_g} = 1$$

$$I_I = I_{g1}$$


$$I_{II} = I_{g2}$$

$$R_{31}I_I + R_{32}I_{II} + R_{33}I_{III} = E_{III}$$

$$R_{33} = R_4 + R_5$$

$$R_{31} = R_5$$

$$R_{32} = 0$$

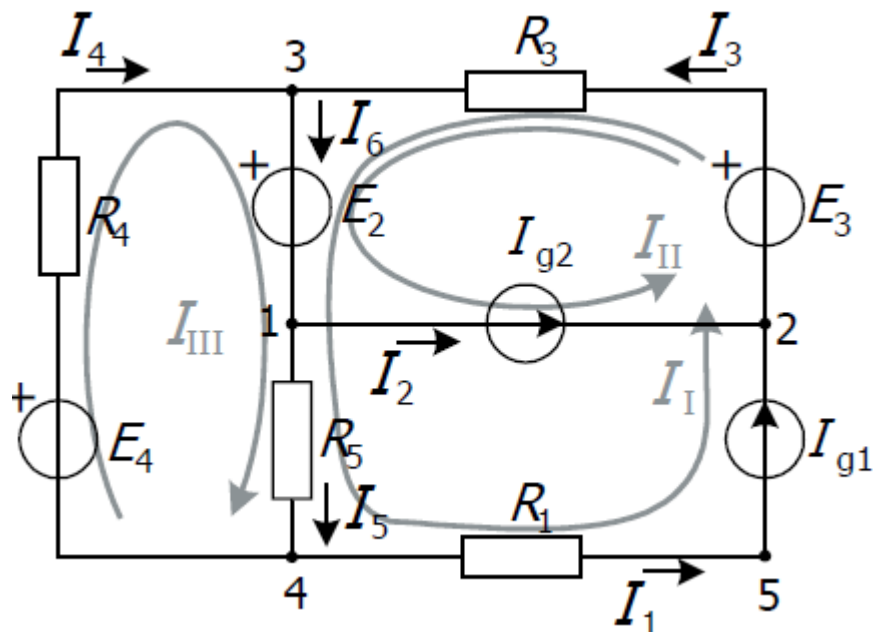



Konturne struje

Zadatak II.8.2.4 a)

$$R_5 I_{g1} + (R_4 + R_5) I_{\text{III}} = E_4 - E_2 \quad \Rightarrow \quad I_{\text{III}} = \frac{E_4 - E_2 - R_5 I_{g1}}{R_4 + R_5} = \frac{-350 \text{ V}}{50 \Omega} = -7 \text{ A}$$

$$I_1 = I_{\text{I}} = I_{g1} = 12 \text{ A},$$


$$I_2 = I_{\text{II}} = I_{g2} = 6 \text{ A},$$

$$I_3 = I_{\text{I}} + I_{\text{II}} = 12 \text{ A} + 6 \text{ A} = 18 \text{ A},$$

$$I_4 = I_{\text{III}} = -7 \text{ A},$$

$$I_5 = I_{\text{I}} + I_{\text{III}} = 12 \text{ A} - 7 \text{ A} = 5 \text{ A},$$
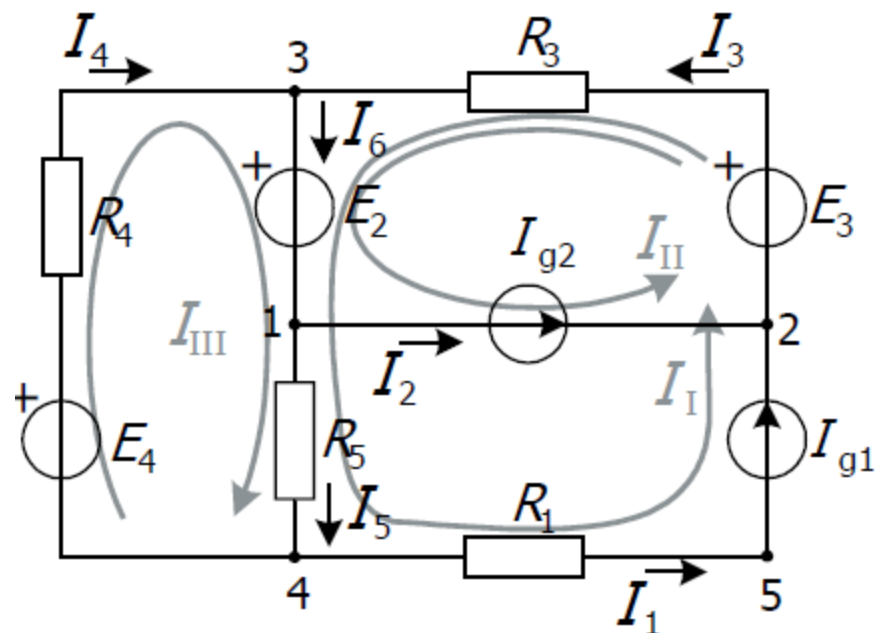
$$I_6 = I_{\text{I}} + I_{\text{II}} + I_{\text{III}} = 12 \text{ A} + 6 \text{ A} - 7 \text{ A} = 11 \text{ A}.$$






Konturne struje

Zadatak II.8.2.4 b)

$$P_{I_{g1}} = U_{25} \cdot I_{g1}$$

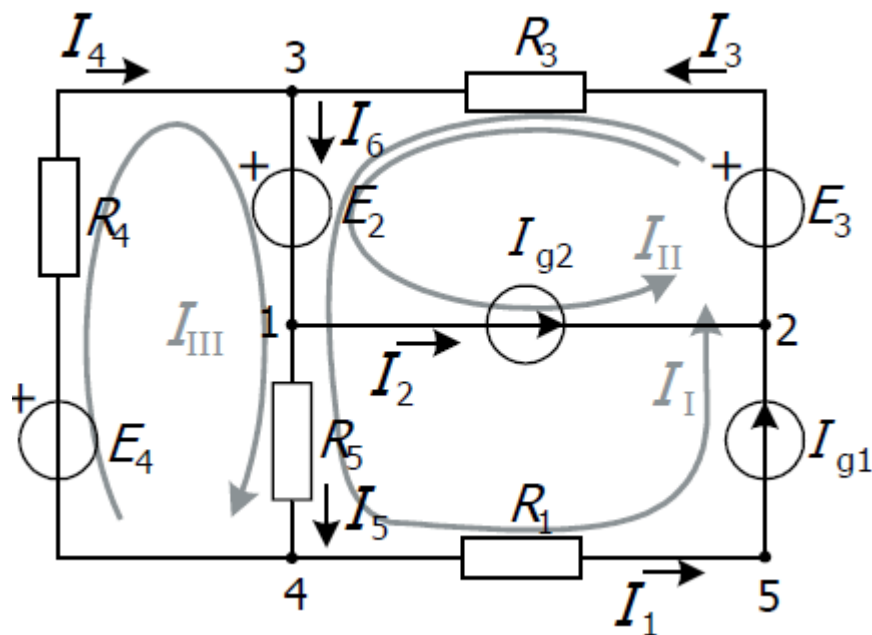

$$U_{25} = R_1 I_1 + R_5 I_5 + E_2 + R_3 I_3 - E_3 = 120 \text{ V} + 150 \text{ V} + 30 \text{ V} + 720 \text{ V} - 20 \text{ V} = 1000 \text{ V}$$

$$\Rightarrow P_{I_{g1}} = U_{25} \cdot I_{g1} = 1000 \text{ V} \cdot 12 \text{ A} = 12000 \text{ W} = 12 \text{ kW}$$



Konturne struje

II.8.2.5 U kolu na slici izračunati:

- a) struje u svim granama kola primenom metode konturnih struja,
- b) snagu strujnog generatora I_{g2} .

Vrednosti elemenata:


$$E_1 = 1 \text{ V}, E_4 = 4 \text{ V}, E_5 = 5 \text{ V},$$

$$E_6 = 6 \text{ V}, E_7 = 7 \text{ V}, E_8 = 8 \text{ V},$$

$$I_{g2} = 2 \text{ A}, I_{g3} = 3 \text{ A},$$

$$R_1 = R_2 = 10 \ \Omega, R_3 = R_4 = R_5 = 20 \ \Omega,$$

$$R_7 = R_8 = 30 \ \Omega.$$

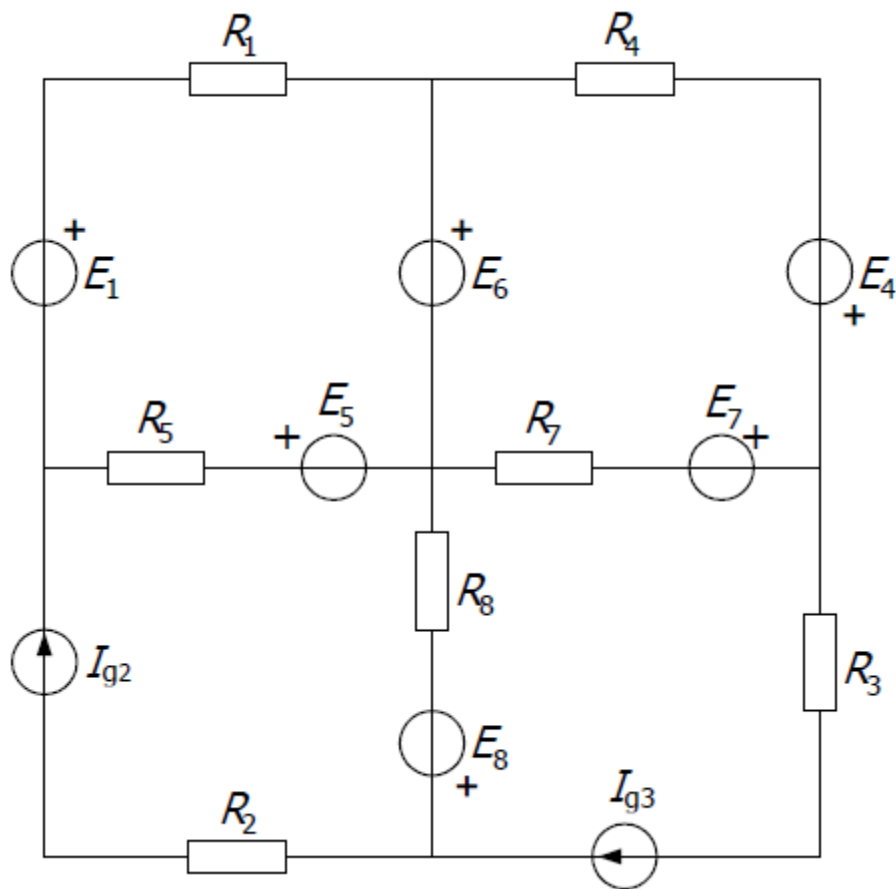



Konturne struje

Zadatak II.8.2.5 a)


$$n_g - (n_{\xi} - 1) - n_{I_g} = 2.$$

$$R_{11}I_I + R_{12}I_{II} + R_{13}I_{III} + R_{14}I_{IV} = E_I$$

$$I_{II} = I_{g2}$$

$$I_{III} = I_{g3}$$
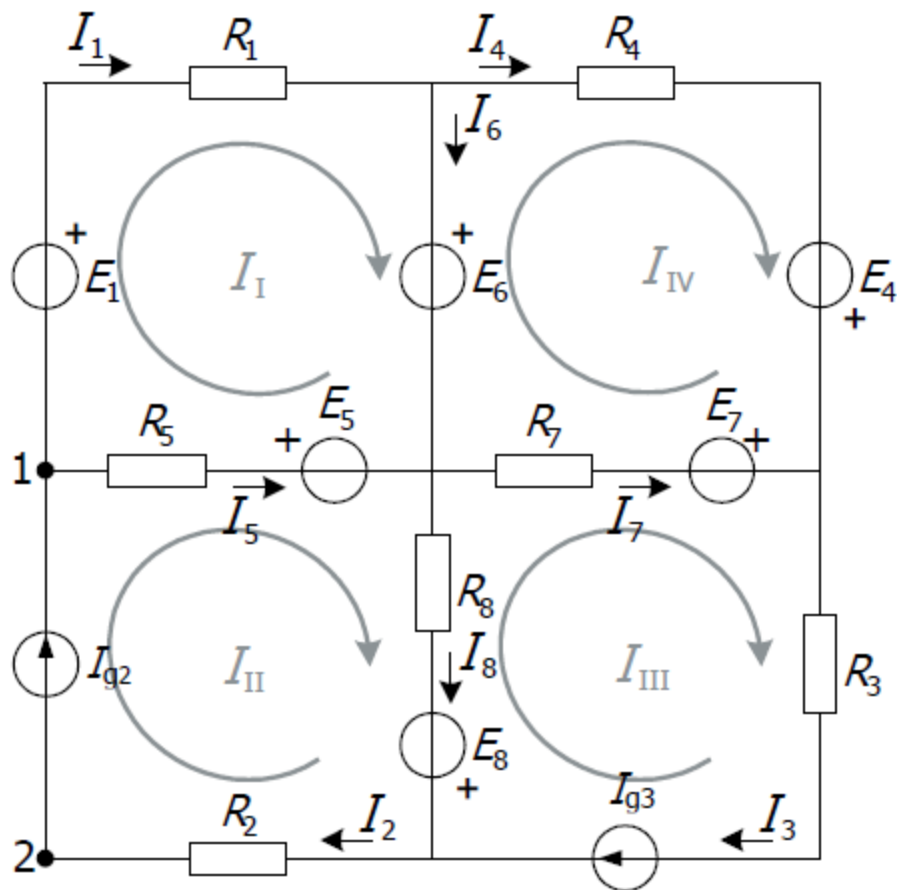
$$R_{41}I_I + R_{42}I_{II} + R_{43}I_{III} + R_{44}I_{IV} = E_{IV}$$





Konturne struje

Zadatak II.8.2.5 a)

$$R_{11} = R_1 + R_5 = 10 \, \Omega + 20 \, \Omega = 30 \, \Omega,$$

$$R_{12} = -R_5 = -20 \, \Omega,$$

$$R_{13} = 0$$

$$R_{14} = R_{41} = 0$$

$$R_{24} = 0$$

$$R_{43} = -R_7 = -30 \, \Omega,$$

$$R_{44} = R_4 + R_7 = 20 \, \Omega + 30 \, \Omega = 50 \, \Omega,$$

$$E_I = E_1 - E_6 + E_5 = 1 \, \text{V} - 6 \, \text{V} + 5 \, \text{V} = 0 \, \text{V},$$

$$E_{IV} = E_6 + E_4 - E_7 = 6 \, \text{V} + 4 \, \text{V} - 7 \, \text{V} = 3 \, \text{V}.$$



Konturne struje

Zadatak II.8.2.5 a)

$$(R_1 + R_5)I_I - R_5 I_{II} = E_1 - E_6 + E_5$$

$$I_{II} = I_{g2}$$

$$I_{III} = I_{g3}$$

$$-R_7 I_{III} + (R_4 + R_7)I_{IV} = E_6 + E_4 - E_7$$

$$(R_1 + R_5)I_I - R_5 I_{g2} = E_1 - E_6 + E_5 \quad \Rightarrow \quad I_I = \frac{E_1 - E_6 + E_5 + R_5 I_{g2}}{R_1 + R_5} = \frac{40 \text{ V}}{30 \Omega} = 1,33 \text{ A}$$

$$-R_7 I_{g3} + (R_4 + R_7)I_{IV} = E_6 + E_4 - E_7 \quad \Rightarrow \quad I_{IV} = \frac{E_6 + E_4 - E_7 + R_7 I_{g3}}{R_4 + R_7} = \frac{93 \text{ V}}{50 \Omega} = 1,86 \text{ A}$$



Konturne struje

Zadatak II.8.2.5 a)

$$I_1 = I_{\text{I}} = 1,33 \text{ A},$$

$$I_2 = I_{\text{II}} = I_{\text{g2}} = 2 \text{ A},$$

$$I_3 = I_{\text{III}} = I_{\text{g3}} = 3 \text{ A}$$


$$I_4 = I_{\text{IV}} = 1,86 \text{ A},$$

$$I_5 = -I_{\text{I}} + I_{\text{II}} = 0,67 \text{ A},$$

$$I_6 = I_{\text{I}} - I_{\text{IV}} = -0,53 \text{ A},$$

$$I_7 = -I_{\text{IV}} + I_{\text{III}} = 1,14 \text{ A},$$
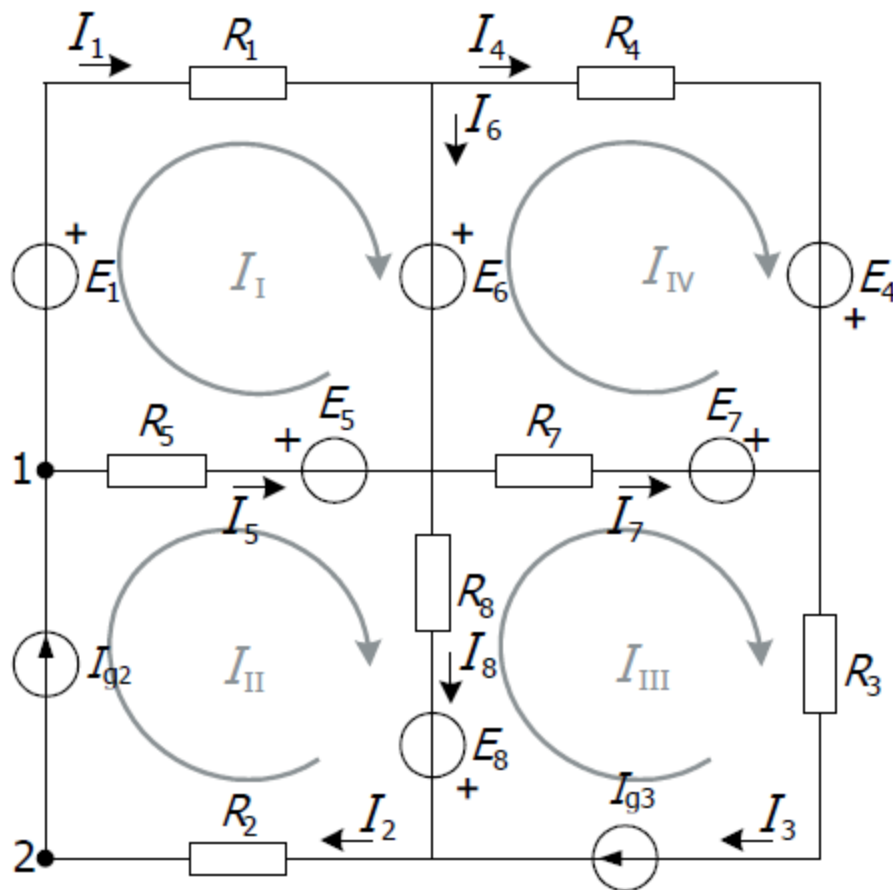
$$I_8 = I_{\text{II}} - I_{\text{III}} = -1 \text{ A}.$$





Konturne struje

Zadatak II.8.2.5 b)

$$U_{12} = R_2 I_2 - E_8 + R_8 I_8 + E_5 + R_5 I_5 = 20 \text{ V} - 8 \text{ V} - 30 \text{ V} + 5 \text{ V} + 13,4 \text{ V} = 0,4 \text{ V}$$

$$P_{I_{g2}} = U_{12} \cdot I_{g2} = 0,4 \text{ V} \cdot 2 \text{ A} = 0,8 \text{ W}$$

