



Elektrotehnika (ASUV)

Vežbe 6

Tevenenova teorema



Tevenenova teorema


Zadatak II.8.4.2

U kolu prikazanom na slici poznata je struja $I_{23} = 50\text{mA}$ kroz otpornik R_4 .
Primenom Tevenenove teoreme odrediti otpornost R_4 , ako je:

$$E_1 = 6\text{V}, E_4 = 40,5\text{V}, E_5 = 5\text{V},$$

$$R_1 = 2\text{k}\Omega, R_2 = 6\text{k}\Omega,$$

$$R_3 = 750\Omega, R_5 = 750\Omega.$$

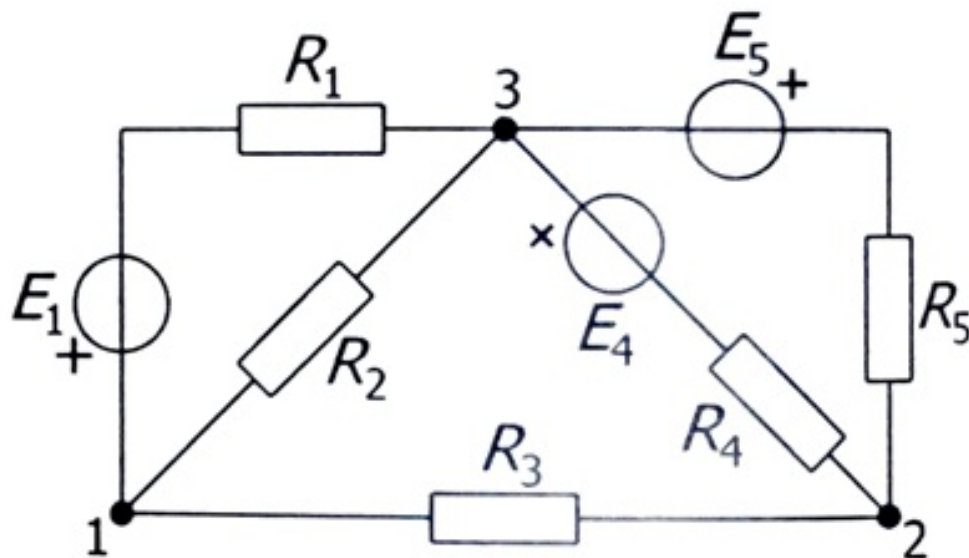




Tevenenova teorema

Zadatak II.8.4.2

Rešenje:

Pošto je poznata struja koja protiče kroz granu sa otpornikom R_4 , tu granu ćemo ukloniti, i ostatak kola predstaviti pomoću Tevenenovog generatora.

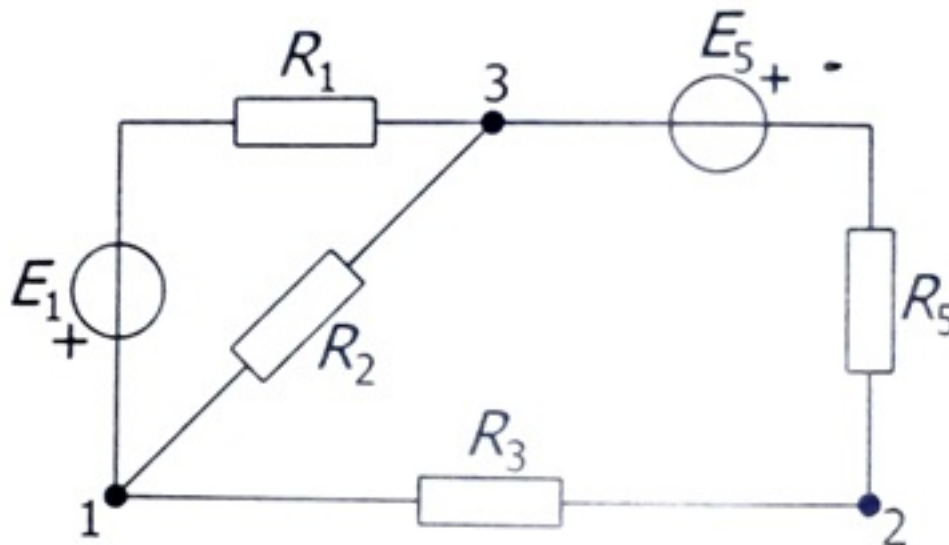Prvo je potrebno pronaći napon Tevenenovog generatora, odnosno napon između tačaka 2 i 3 u kolu.






Tevenenova teorema

Zadatak II.8.4.2

Rešenje:

Da bi odredili napon između tačaka 2 i 3, prvo je potrebno da pojednostavnimo kolo transfiguracijom generatora.
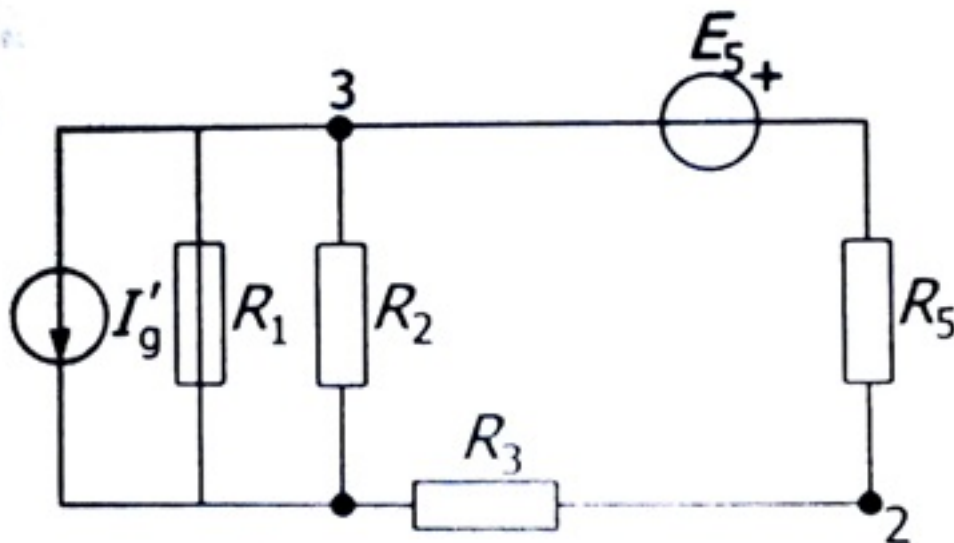
$$I'_g = \frac{E_1}{R_1} = \frac{6V}{2k\Omega} = 3mA$$






Tevenenova teorema

Zadatak II.8.4.2

Rešenje:

Otpornoci R_1 i R_2 vezani su paralelno:

$$R_{12} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = 1.5k\Omega$$

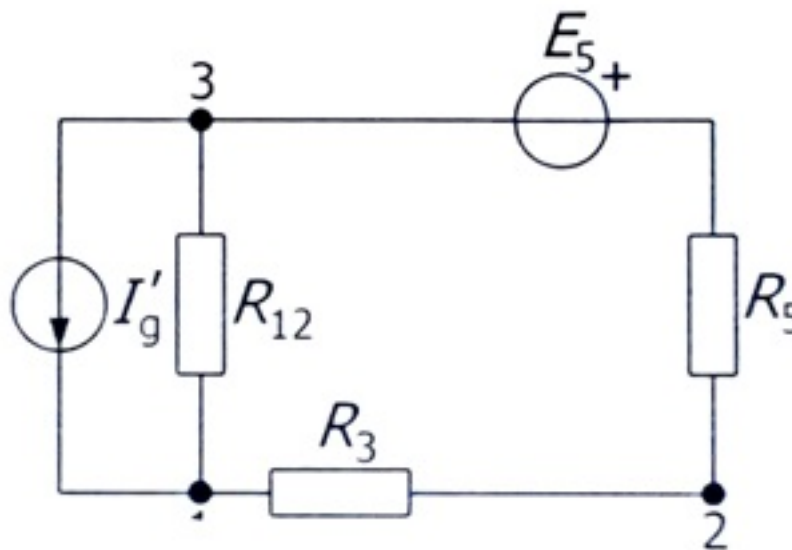



Tevenenova teorema

Zadatak II.8.4.2

Rešenje:


Ponovo primenjujemo transfiguraciju generatora:

$$E'' = R_{12}I_g' = 1.5k\Omega \cdot 3mA = 4.5V$$

zatim primenom Omovog zakona na prosto kolo računamo struju I

$$I = \frac{E_5 - E''}{R_{12} + R_3 + R_5} = \frac{36V}{3k\Omega} = 12mA$$

$$E_T = U_{23}|_{OK} = E_5 - R_5I = 31.5V$$

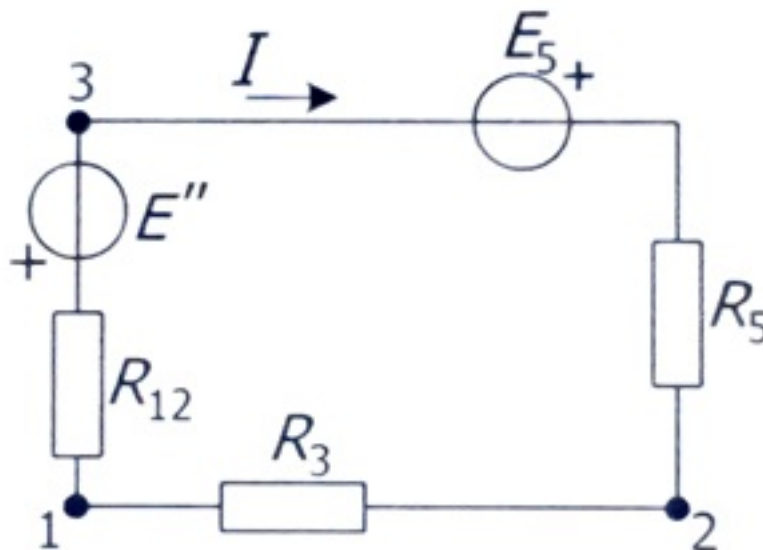




Tevenenova teorema

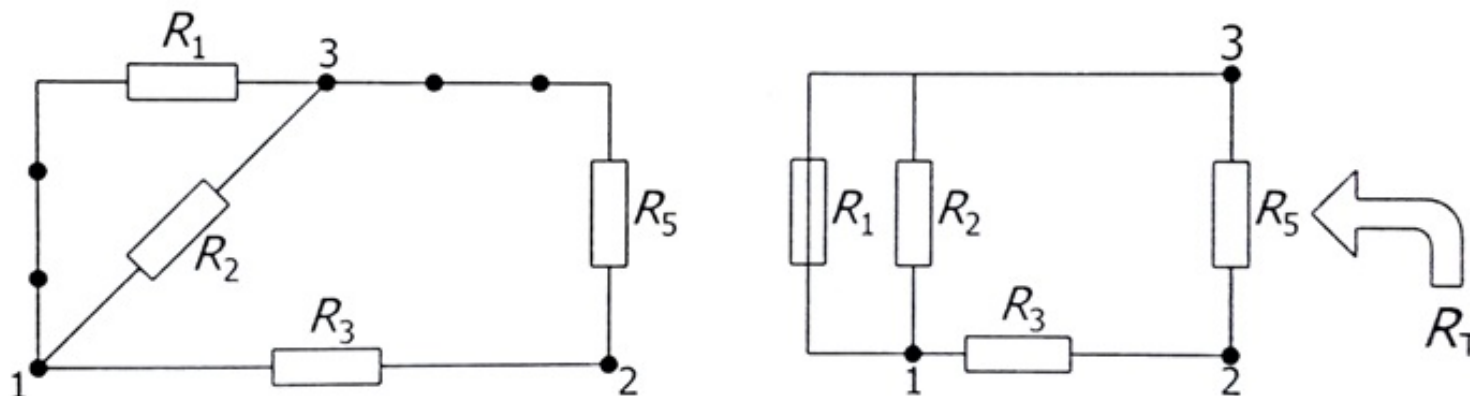Zadatak II.8.4.2

Rešenje:

Potrebno je još pronaći otpornost Tevenenovog generatora:



$$R_T = ((R_1 || R_2) + R_3) || R_5 = \frac{\left(\frac{R_1 R_2}{R_1 + R_2} + R_3\right) R_5}{\frac{R_1 R_2}{R_1 + R_2} + R_3 + R_5} = 562.5 \Omega$$



Tevenenova teorema

Zadatak II.8.4.2

Rešenje:


Sada imamo jednostavno kolo:

Pa je prema Omovom zakonu

$$I_{23} = \frac{E_T + E_4}{R_T + R_4}$$

pa je nepoznata otpornost:
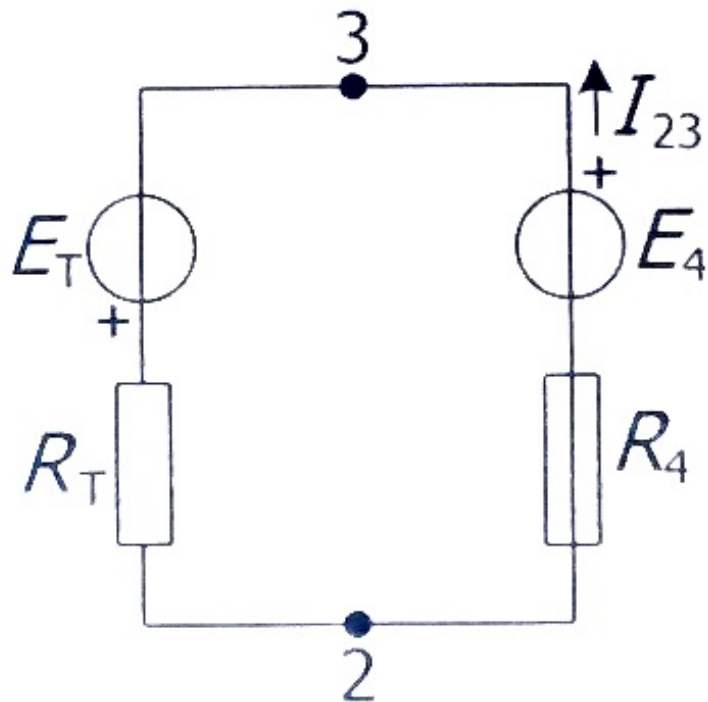
$$R_4 = \frac{E_T + E_4}{I_{23}} - R_T = 730\Omega - 562.5\Omega = 167.5\Omega$$





Prilagođenje prijemnika po snazi


II.8.4.1.1 U kolu sa slike poznato je:

$$R_1 = 20 \, \Omega, R_2 = 10 \, \Omega,$$

$$R_3 = 10 \, \Omega, R_4 = 5 \, \Omega,$$

$$I_{g1} = 2,6 \, \text{A}$$



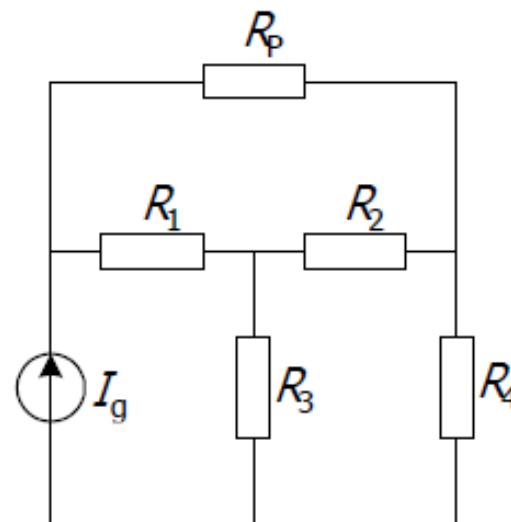
Odrediti otpornost prijemnika R_p tako da se na njemu razvija maksimalna snaga. Kolika je ta snaga?





Prilagođenje prijemnika po snazi

Zadatak II.8.4.1.1 Određivanje R_T

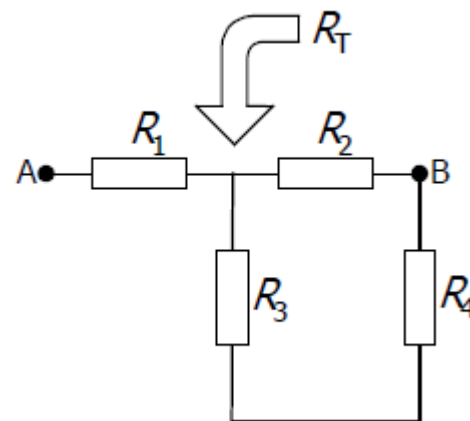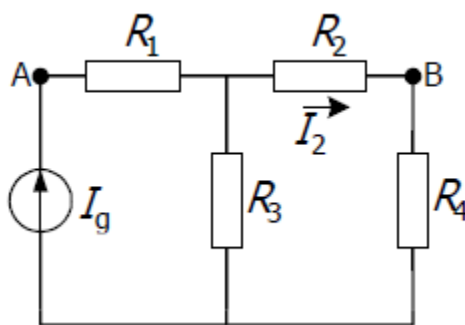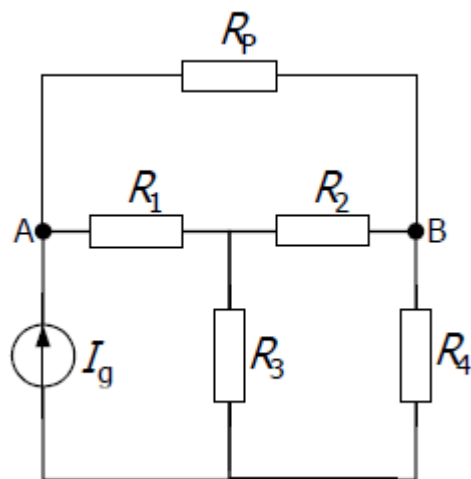


$$R_T = (R_3 + R_4) \parallel R_2 + R_1 = \frac{(R_3 + R_4)R_2}{R_3 + R_4 + R_2} + R_1 = 26 \, \Omega$$

$$R_p = R_T = 26 \, \Omega$$




Prilagođenje prijemnika po snazi

Zadatak II.8.4.1.1 Određivanje E_T

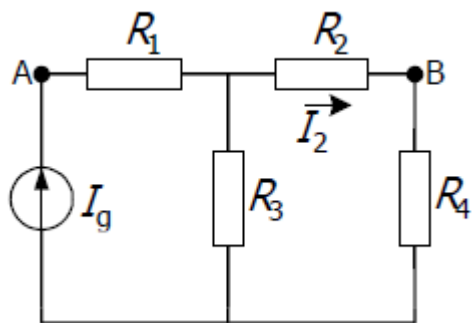

$$I_2 = \frac{R_3 + R_4}{R_2 + R_3 + R_4} I_g = \frac{15 \Omega}{25 \Omega} \cdot 2,6 \text{ A} = 1,56 \text{ A}$$

$$E_T = U_{AB} \Big|_{OK} = R_2 I_2 + R_1 I_g = 67,6 \text{ V}$$

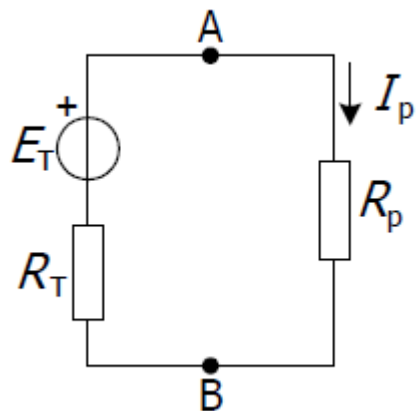

$$I_p = \frac{E_T}{R_T + R_p} = \frac{67,6 \text{ V}}{52 \Omega} = 1,3 \text{ A}$$

$$P_{R_p} = I_p^2 R_p = 43,94 \text{ W}$$




Prilagođenje prijemnika po snazi

II.8.4.1.2 U kolu prikazanom na slici odrediti otpornost otpornika R_3 tako da se na njemu razvije maksimalna snaga. Odrediti tu snagu.

$$E_1 = 10 \text{ V}, E_5 = 100 \text{ V},$$

$$R_1 = 2 \text{ } \Omega, R_2 = 40 \text{ } \Omega,$$


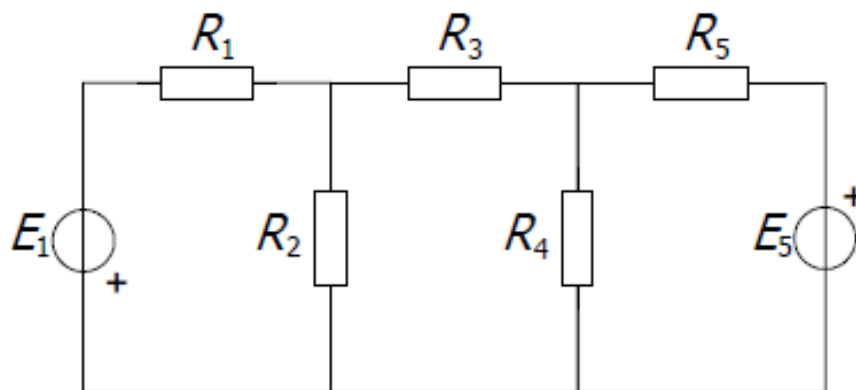
$$R_4 = 20 \text{ } \Omega, R_5 = 20 \text{ } \Omega$$





Prilagođenje prijemnika po snazi

Zadatak II.8.4.1.2

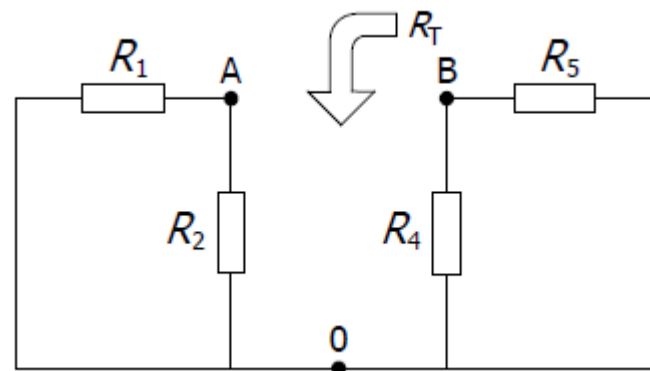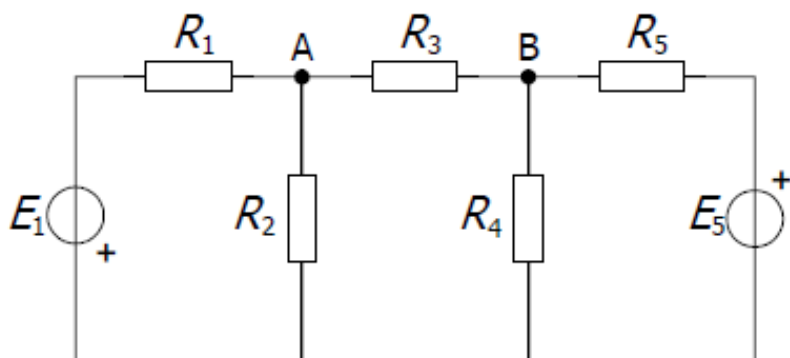

$$R_T = (R_1 \parallel R_2) + (R_4 \parallel R_5) = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_4 R_5}{R_4 + R_5} = 1,9 \Omega + 10 \Omega = 11,9 \Omega$$

$$R_p = R_T = 11,9 \Omega$$




Prilagođenje prijemnika po snazi

Zadatak II.8.4.1.2

$$I_1 = \frac{E_1}{R_1 + R_2} = \frac{10 \text{ V}}{42 \Omega} = 0,24 \text{ A}$$

$$I_2 = \frac{E_5}{R_4 + R_5} = \frac{100 \text{ V}}{40 \Omega} = 2,5 \text{ A}$$

$$E_T = U_{AB} \Big|_{OK} = U_{OB} + U_{AO} = -R_4 I_2 - R_2 I_1 = -59,6 \text{ V}$$

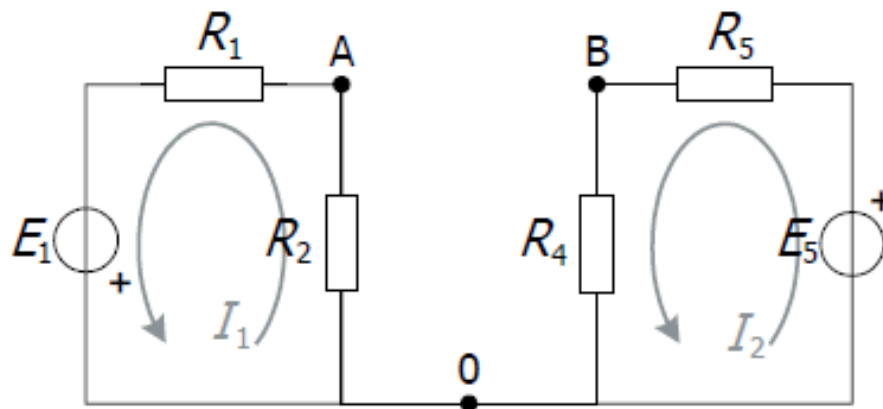



Prilagođenje prijemnika po snazi

Zadatak II.8.4.1.2

$$I_p = \frac{E_T}{R_T + R_p} = \frac{-59,6 \text{ V}}{23,8 \Omega} = -2,5 \text{ A}$$

$$P_{R_p} = I_p^2 R_p = 74,375 \text{ W}$$

